

Greatest Common Divisor

1. Synopsis:

The purpose of this lab is to teach RTL design as well as some techniques in the “top” design. Here, we take two 8-bit unsigned numbers and calculate their greatest common divisor (GCD). You will implement Euclid’s Algorithm for computing GCD as a Mealy machine using one-hot state encoding. We will then implement the design on Xilinx Spartan 3E FPGA board. The key idea in this lab is to learn RTL method of design in Verilog (state machine design and data path design in Verilog) and also understanding single-stepping and Virtual I/O.

2. Introduction:

In this lab, you will explore implementing a popular algorithm for computing greatest common divisor (GCD).

Prelab: If the GCD algorithm was not discussed in your class, please watch the webcast on “Small system design example - GCD” posted at <http://denecs.usc.edu/hosted/puvvada/EE201L.htm> . Before coming to the lab you are required to complete the state diagram provided in the prelab.

Part 1: In part 1 you will implement the core design in Verilog, create a test fixture, and simulate using Modelsim.

Part 2: In part 2 you are provided with an incomplete top level design with a number of TODO sections. These include exercising single-step clock enable control. You will complete the top level design, download to the board, and verify the results.

Part 3: In part 3, you are given a completed top design with added “Virtual I/O” for you to read and understand. This is based on an earlier example design of a divider with “Virtual I/O”. A number of sections were specifically marked with questions for you to answer and demonstrate your understanding of the given design.

Part 4: Here some aspects of the top design (particularly the Virtual I/O aspects) are changed. You will revise earlier top from Part 3, implement your design using this top, download to the board, and test.

When you finish this lab, you are expected to be confident in RTL coding of any given core task and designing a suitable top including Virtual I/O to go with the core.

3. Algorithm:


Following is the Euclid’s algorithm to compute GCD of two numbers, A and B. The algorithm was reported by J. Stein in 1967 and is available on the web at <http://www.nist.gov/dads/HTML/binaryGCD.html> (link is perhaps inactive) and also at http://en.wikipedia.org/wiki/Binary_GCD_algorithm.

1. if $A = B$, then $\text{GCD}(A,B) = A$
2. else if A is less than B , swap A and B
3. else if A and B are even, then $\text{GCD}(A,B) = 2 \times \text{GCD}(A/2,B/2)$
4. else if A is odd and B is even, then $\text{GCD}(A,B) = \text{GCD}(A,B/2)$
5. else if A is even and B is odd, then $\text{GCD}(A,B) = \text{GCD}(A/2,B)$
6. else if both are odd, then $\text{GCD}(A,B) = \text{GCD}((A-B),B)$

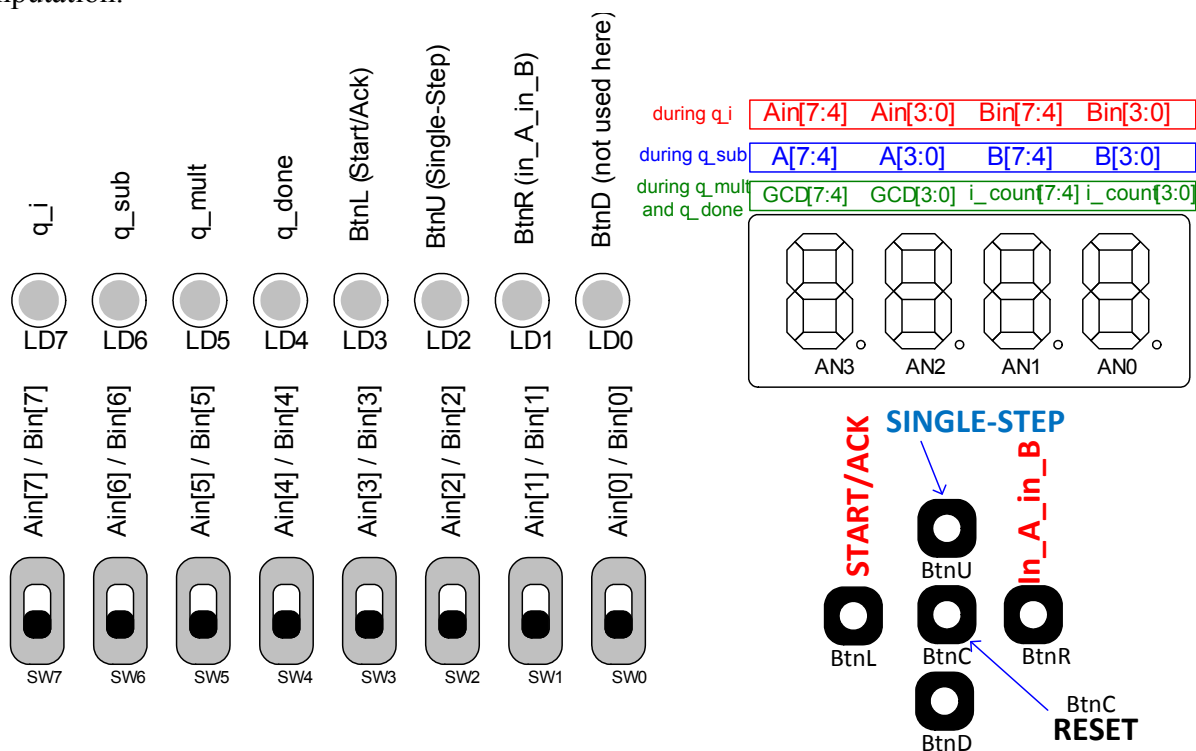4. Description of the circuit:

In this design, you will implement a state machine along with a data path unit. This circuit will compute the greatest common divisor of two 8-bit unsigned numbers, **A** and **B**, and output the **GCD** as the result. The eight switches on the board are used to enter the two numbers, one at a time. The core design will compute the **GCD** when signalled to start and output the result for displaying on the seven segment display.

At **RESET** the machine goes to **INITIAL** state and awaits insertion of **A** and **B**. At the *first* press of **BtnR** the value on the switches will be stored as **Ain** in the *top*, and at the *second* press of the same button, **BtnR**, the value on the switches will be stored as **Bin** in the *top*. These two values will be displayed on the seven segment display. **SSD3** and **SSD2** show the two digits of **Ain** and **SSD1** and **SSD0** show the two digits of **Bin**. **BtnL** is used to signal the state machine to **START** the computation. Four LEDs, **LD7-LD4**, indicate the current state of the state machine. When the computation is completed, the value of **A** and **B** on the seven segment display will be replaced by the result of computation. **SSD3** and **SSD2** will be used to show the two digits of the **GCD** of **A** and **B**. **BtnL** (which was used to signal **START**) is also used to signal acknowledging of noticing the results of the completed computation.



5. Prelab:

- Q 5. 1: Note that in the top level design, we use a `hex-to-ssd` conversion unit to convert the 4-bit binary numbers to their corresponding seven segment code, which is then sent to one of the **SSDs**. In this **GCD** design, **A**, **B** and **GCD** are 8-bit numbers, instead of 4-bit numbers. To show a 8-bit numbers on a pair of **SSDs** do you think we display the numbers in hex digits or decimal (**BCD**)? (2 pts)

To display on 4 **SSDs**, are you using four `hex-to-ssd` conversion units, or ...(2 pts)

- Q 5. 2: Follow the Euclid's algorithm and compute the GCD of the following pairs of numbers. Report your step by step computation.(6 pts = 3 + 3)

(a) GCD(36,24)

State: Initial A = 36 B = 24 i = 0

State: Sub A = B = i =

State: A = B = i =

State: A = B = i =

State: A = B = i =

State: A = B = i =

State: A = B = i =

State: GCD = i =

State: GCD = i =

State: GCD = i =

(b) GCD(5, 15):

State: Initial $A = 5$ $B = 15$ $i = 0$

State: $A =$ $B =$ $i =$


State: $A =$ $B =$ $i =$

State: $A =$ $B =$ $i =$

State: $A =$ $B =$ $i =$

State: GCD = $i =$

 Q 5. 3: If GCD was not discussed in class, please watch the webcast, “Small System Design Example -- GCD” at <http://denecs.usc.edu/hosted/puvvada/EE201L.htm>. Understand the state machine of the GCD computation thoroughly and complete the following state diagram.(5 pts)



6. Procedure:

Part 0: Preview the completed design

6.1 Download two zip files ee201L_GCD.zip and ee201L_GCD_VIO.zip. Extract them to form two directories ee201L_GCD and ee201L_GCD_VIO under your C:\Xilinx_projects. Open the subdirectory ee201L_GCD. Download the bit file TAs_ee201_gcd_top.bit to your Nexys 3 board. Operate the switches and buttons and observe LEDs and SSDs to see how your design will behave when completed for the following Ain and Bin.

Ain = 60 (00111100) = 3C hex and Bin = 84 (01010100) = 54 hex.

LD7 is on to indicate **q_i** state

1. on reset 0 0 0 0 Ain, Bin
 2. set sw[7:0] = 00111100
and press BtnR (in_AB_pulse) 3 C 0 0 Ain, Bin
 3. set sw[7:0] = 01010100
and press BtnR (in_AB_pulse) 3 C 5 4 Ain, Bin
- Until now we are in **q_i** state and LD7 is on. Observe that we now move to **q_sub** state and the LD6 glows.
4. press BtnL (start_ack)
to start 3 C 5 4 A, B
 5. press BtnU to single-step 5 4 3 C A, B swapped
 6. press BtnU to single-step 2 A 1 E A, B halved, i = 1
 7. press BtnU to single-step 1 5 0 F A, B halved, i = 2
 8. press BtnU to single-step 0 6 0 F A-B, B
 9. press BtnU to single-step 0 F 0 6 A, B swapped
 10. press BtnU to single-step 0 F 0 3 A, B/2
 11. press BtnU to single-step 0 C 0 3 A-B, B
 12. press BtnU to single-step 0 6 0 3 A/2, B
 13. press BtnU to single-step 0 3 0 3 A/2, B

Until now we are in **q_sub** state and LD6 is on.

Observe that we now move to **q_mult** state and the LD5 glows.


14. press BtnU to single-step 0 3 0 2 GCD, i_count
15. press BtnU to single-step 0 6 0 1 GCD, i_count

Until now we are in **q_mult** state and LD5 is on.

Observe that we now move to **q_done** state and the LD4 glows.

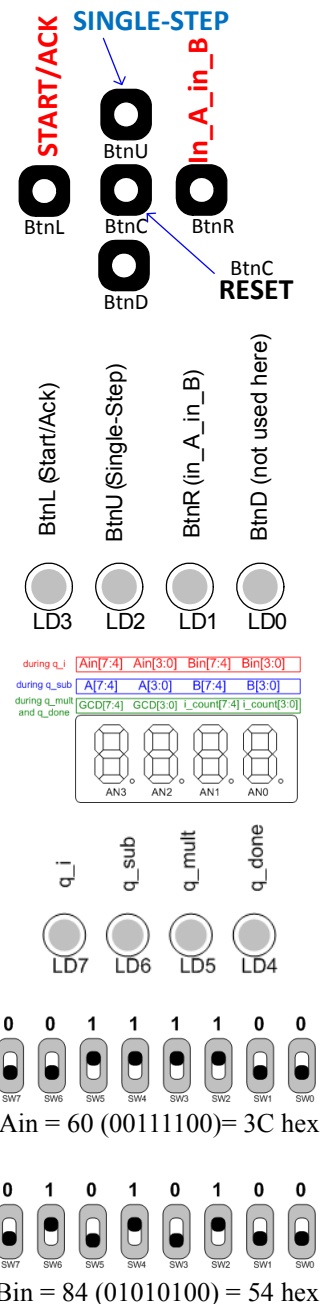16. press BtnU to single-step 0 C 0 0 GCD, i_count
17. press BtnU to single-step <= nothing new happens as the state machine is waiting for ACK.
18. press BtnL (start_ack)
to ACK 3 C 5 4 Ain, Bin

Now we are back in **q_i** state and LD7 glows.



Note: The .bit files provided by us bear “TAs_” prefix. They have the dot points on SSDs lit to differentiate from the .bit files created by the students.

6.2 Also, please go through the **divider_verilog** design example provided to you separately along with the associated webcasts.

Part 1: Core design and simulation

6.3 In the prelab you have downloaded two zip files `ee201L_GCD.zip` and `ee201L_GCD_VIO.zip` and extracted them to form two directories `ee201L_GCD` and `ee201L_GCD_VIO` under your `C:\Xilinx_projects`. Each of these two subdirectories deals with two parts of this lab: `ee201L_GCD` deals with parts 1 and 2 of this lab and `ee201L_GCD_VIO` deals with parts 3 and 4 of this lab.

6.4 Open the directory `ee201L_GCD`. Open the core design file `ee201_GCD.v` (in Notepad++ preferably). This (`ee201_GCD.v`) is a ‘bare bones’ module for the GCD core design. Use this file to implement the state machine you completed in the prelab along with the required data path. Recall that the control unit and data path can be coded in the same `always` block. Follow the guidelines below when coding your state machine.

- Name your `always` and initial blocks. It makes debugging easier. After begin type a colon (`:`) and give a name as shown.

```
always @ (posedge Clk, posedge Reset)
  begin : my_GCD
```
- Data registers, which usually need not be initialized at reset, should be assigned X’s at reset in order to avoid the tool from inferring an unnecessary re-circulating multiplexer with each such register.

```
if (Reset)
  begin
    state <= I;
    i_count <= 8'bxx;
    A <= 8'bxx;
    B <= 8'bxx;
    AB_GCD <= 8'bxx;
  end
```
- Although we are coding data path unit together with the control unit, you should separate state transitions from data transitions by suitable comments to make it more readable.

6.5 Once you have completed the core design, open the test fixture, `ee201_GCD_tb.v`, and complete the missing lines. To do so, you are required to compute the *minimum* amount of wait time required for each set of inputs (hint: minimum wait time for each set of inputs depends upon the number of cycles it will take your state machine to compute the GCD for that specific input data set). Compare the results of your simulation with the prelab and show your waveforms to your TA.

Part 2: Top-level design

This top design is based on the top design for the divider design example presented to you earlier.

6.6 As a first step, get acquainted with the debouncer design. Refer to the section on debouncer and single-stepping in the handout on an example design of a divider provided to you earlier. Please read the state diagram for the debouncer and also read the code `ee201_debounce_DPB_SCEN_CCEN_MCEN_r1.v`. Test the debouncer by simulating it in modelsim using the testbench `ee201_debounce_DPB_SCEN_CCEN_MCEN_tb_r1.v` for **40 us**. We recommend that you close the waveform window produced automatically for you, type `restart` at `vsim>` prompt and invoke the `.do` file provided to you: `do ee201_debounce_DPB_SCEN_CCEN_MCEN_tb_wave.do`. Please zoom into the first **1 us** and then zoom in to the first **17us** to notice its behavior.


Notice that, in this revised code `ee201_debounce_DPB_SCEN_CCEN_MCEN_r1.v`, we have increased the time gap between consecutive **MCEN** pulses to **1.342 sec**.

6.7 Read the following two top designs of the divider example design:

`divider_top_with_debounce.v` and `divider_top_with_single_step.v`.

 6.8 Suppose we combine both the above TOP designs together to make one TOP called, say, `divider_top_with_debounce_and_single_step.v`. And, say, the button assignment is as shown on the side. Then the instantiation lines responsible (a) for generating single-clock wide pulses for **Start_Ack_SCEN** to work as the **START** signal and also the **ACK** signal and (b) for generating the **SCEN** signal to work as single-step-control signal, would look like this:

`divider_top_with_debounce_and_single_step.v`
(combination of two given designs)



```
ee201_debouncer #(.N_dc(25)) ee201_debouncer_2
    (.CLK(sys_clk), .RESET(Reset), .PB(BtnL), .DPB( ),
     .SCEN(Start_Ack_SCEN), .MCEN( ), .CCEN( ));

ee201_debouncer #(.N_dc(25)) ee201_debouncer_0
    (.CLK(sys_clk), .RESET(Reset), .PB(BtnU), .DPB( ),
     .SCEN(SCEN), .MCEN( ), .CCEN( ));


// instantiate the core divider design. Note the .SCEN(SCEN)
divider divider_1(.Xin(Xin), .Yin(Yin), .Start(Start_Ack_SCEN),
    .Ack(Start_Ack_SCEN), .Clk(sys_clk), .Reset(Reset),
    .SCEN(SCEN), .Done(Done), .Quotient(Quotient),
    .Remainder(Remainder), .Qi(Qi), .Qc(Qc), .Qd(Qd) );
```

We encourage you to take 30 minutes *at home* (not in lab) to actually create the “`divider_top_with_debounce_and_single_step.v`”, synthesize, and test it on your Nexys-3.


The debouncer design here (in the GCD design) may be slightly different from the debouncer design given with the divider design. Here (in `_r1` version), we have increased the time gap between consecutive **MCEN** pulses to **1.342 sec**. Hence instantiations of the debouncer similar to the above will use here an `N_dc` parameter of 28: `ee201_debouncer #(.N_dc(28)) ee201_debouncer_2`

 6.9 In our `ee201_GCD_top.v`, we intend to use **BtnL** and **BtnU** in a fashion similar to the above divider design.

In addition, we use **BtnR** for depositing **Ain** and **Bin** in two registers in the *top* (note: in the *top*, not in the *core*) called **Ain** and **Bin**. We have only 8 switches on the Nexys-3 board. But we need to provide two 8-bit operands to the core design. So we have two registers, called **Ain** and **Bin** in the *top* design, and we deposit an 8-bit value from the switches into one of these two registers, one at a time. We set **Ain** value on the switches, press **BtnR** once. Then set the **Bin** value on the switches, press **BtnR** the second time. This requires that we have a flip-flop to remember if the **BtnR** was pressed once already. So we declared a FF (`reg A_bar_slash_B;`), initialized it under reset (`A_bar_slash_B <= 1'b0;`), and toggled it (`A_bar_slash_B <= ~ A_bar_slash_B;`) every time the **BtnR** was pressed. So, do you think you can use the *bare* **BtnR** signal for toggling or do you need to debounce and produce a single-clock-wide pulse, called, say, `in_AB_Pulse`? Read the incomplete `ee201_GCD_top.v` and complete the “TODO” section related to this. We have a number of “TODO” sections in `ee201_GCD_top.v` for you to complete. Use search/find function in your editor to locate them.



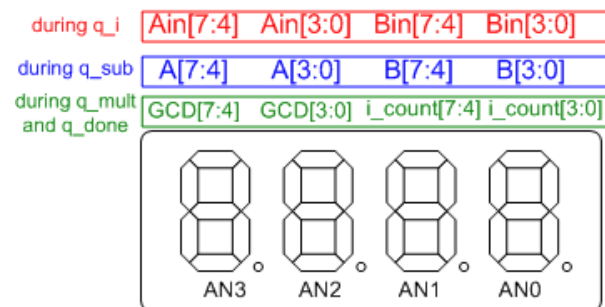6.10 In another “TODO” section, you are required to write a small piece of code that will assign different values to the SSDs depending on the current state. In the initial state, the SSDs will display the **Ain** and **Bin** being conveyed to the core design. These are the values *deposited* in the **Ain** and **Bin** registers (and not the *raw* values of the switches. In the subtract state, the SSDs will display the changing values of **A** and **B**. In the multiply and done states, the SSDs will display the **GCD** value and 2’s counter value.



To assign data values to the SSD, you can use the conditional continuous assignment operator (also known as tertiary assignment operator) as shown in the example below (this implements a 2:1 mux):

```
assign y = s ? i1 : i0;
```

Note: You can define a 4 to 1 mux using a nested operations. looking like:

```
assign y = s1 ? (s0 ? i3: i2): (s0 ? i1: i0);
```

6.11 Make sure that you do not display dot points on the SSDs. This is to differentiate your .bit file from the TA’s .bit file!


6.12 After having completed all “TODO” section in the top design, synthesize, implement, and download your design to the board. Demonstrate it to your TA. Celebrate your success!!!

Part 3: Understanding a revised TOP design incorporating multi-stepping and Virtual I/O


- 6.13 Open the directory `ee201L_GCD_VIO`. Here, we made two changes to the top design:
- replace the **SCEN** with **MCEN**,
 - add Virtual I/O so that I/O can be conducted from the Adept I/O Ex GUI

6.14 This part of the lab is to reaffirm your understanding of the Virtual I/O. *There is no code to write or fill-in.* You need to read the TOP design file (`ee201_GCD_top_VIO.v`) and understand. Before reading this file, first watch the webcasts related to VIO, posted for the divider design example. There are a few sections marked as “TODO”. Read these sections specifically and answer the questions posed.

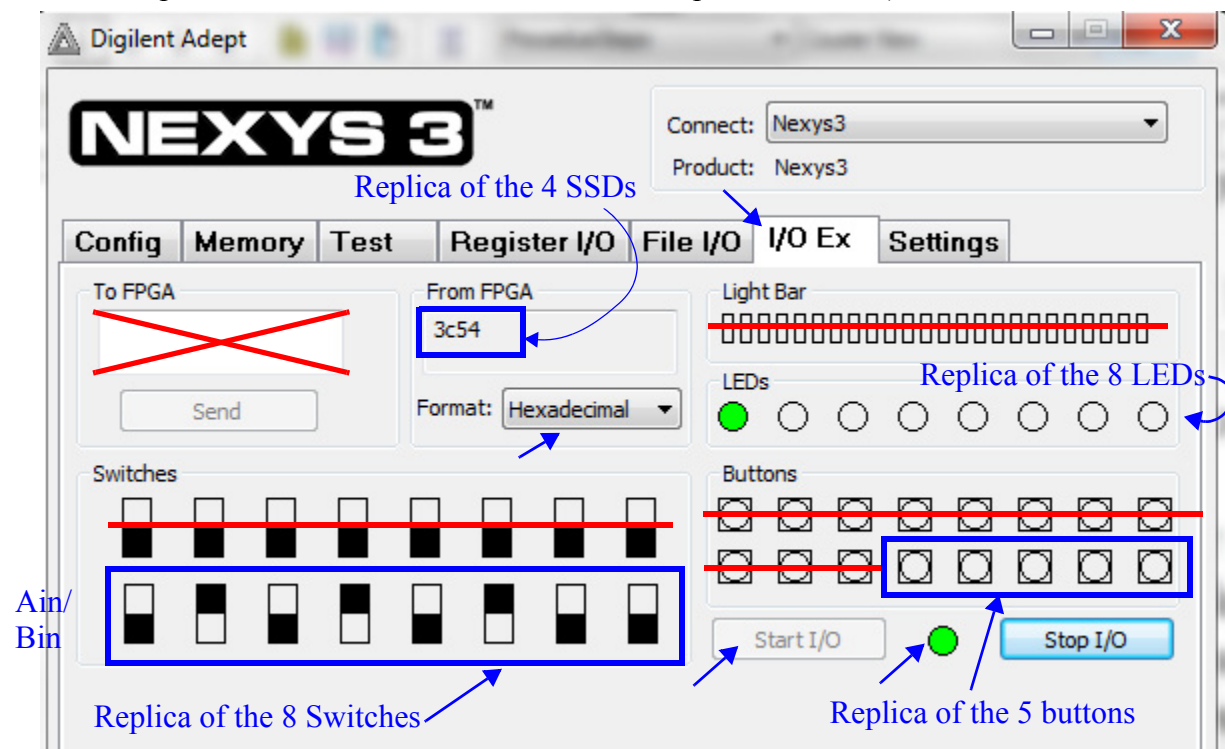- 6.15 Adept Virtual I/O resource utilization for this part of the lab (unused resources are crossed out):




The push button mapping is as follows:

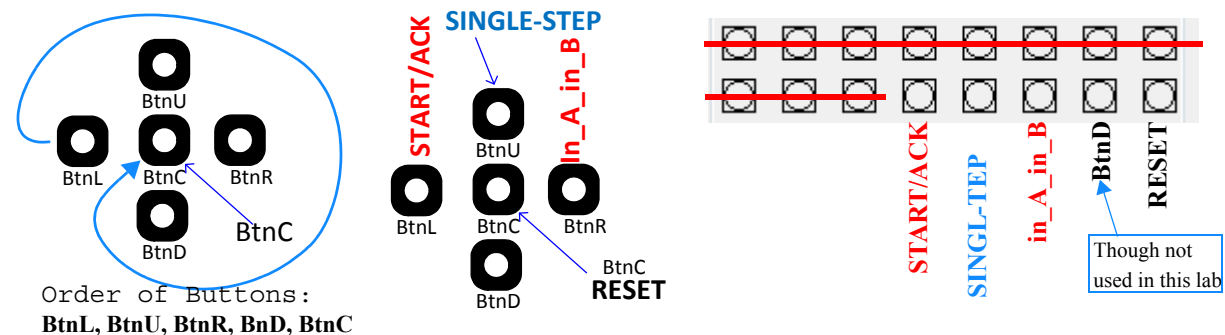

- 6.16 Download the bit file `TAs_ee201_gcd_top_vio.bit` and test VIO operation. Please read and understand the `ee201_GCD_top_VIO.v`. Search for the sections marked with “TODO”. Some questions are included in these sections. Arrive at your answers and discuss with your TA. *No written report is needed for this part. Celebrate your success!!!*

Part 4: Revising the TOP design to change some Virtual I/O resource usage

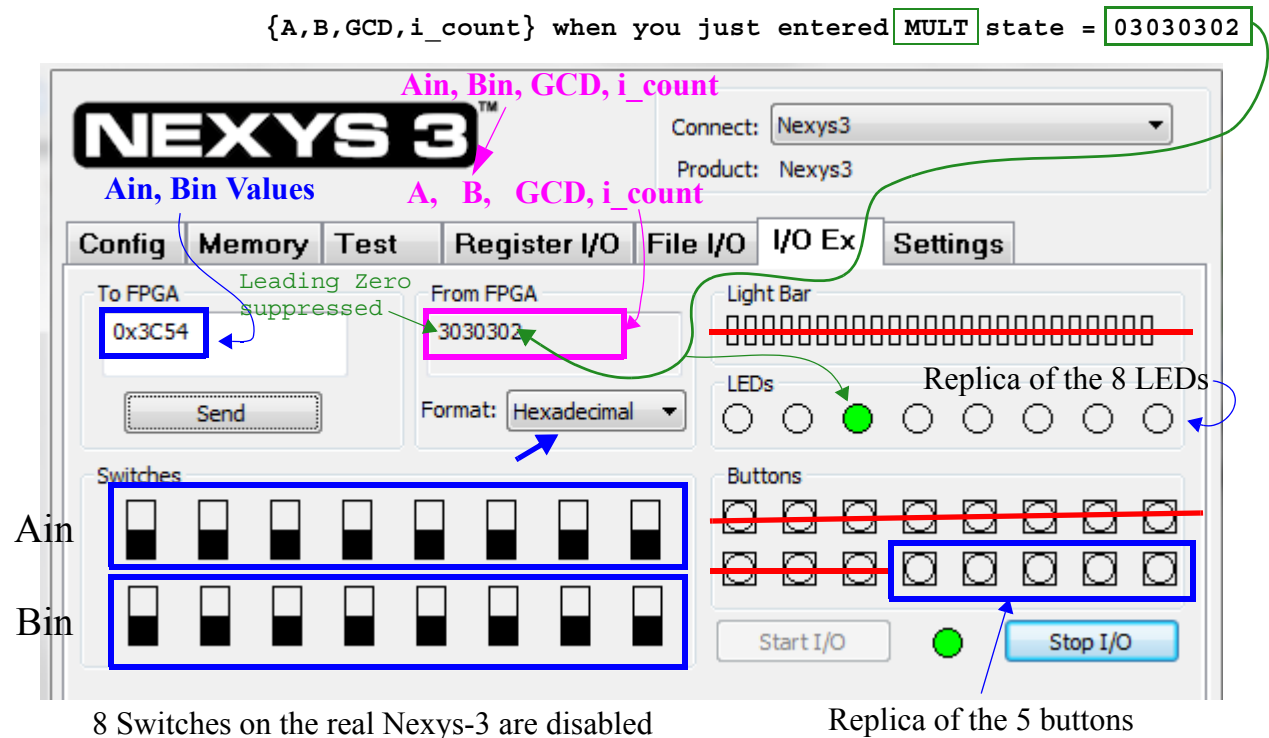6.17 Here, we want you to modify the top design as per the diagram below:




6.18 Make a directory called ee201L_GCD_VIO_Part_4 under your C:\Xilinx_projects. Copy source files (.v and .ucf files) from the ee201L_GCD_VIO directory to this directory. Rename ee201_GCD_top_VIO.v as ee201_GCD_top_Part_4_VIO.v but leave the module name as is (ee201_GCD_top_VIO). Here we do **not** use the 8 switches on the Nexys-3 board for inputting Ain/Bin. We remove the Ain/Bin registers in the TOP design and the BtnR function (in A_in_B) to deposit Ain or Bin, one at a time. We use the 16 switches on the Adept VIO to convey 8-bit Ain and 8-bit Bin to the GCD core design. We also provide for sending 16-bit data alternatively by using the “To FPGA” box facility. We were (in Part 3) merely displaying the 4-digit SSD display on the Nexys-3 board in the “from FPGA” box. In this part (Part 4), we improve the display by showing all the four 8-bit items in the “from FPGA” box:

in the **initial state** (Ain, Bin, AB_GCD, i_count) and

in the **rest of the states** (A, B, AB_GCD, i_count).

```
assign dwIn = q_I ? {Ain_from_VIO, Bin_from_VIO, AB_GCD, i_count} : { A, B, AB_GCD, i_count};
```

 Download the given bit file, TAS_ee201_GCD_top_Part_4_VIO.bit and note the behavior.



Example display in the last clock in Subtract state. In Mult and Done states, we expect A and B to show as both three (303 meaning 0303), but if you performed the harmless operation, $A \leq A - B$; in the last clock in the subtract state, you would see just (3 for 0003) for A and B. It means A became zero.

6.19 Edit your ee201_GCD_top_Part_4_VIO.v to satisfy the above requirements. Implement and test your design. Demonstrate to your TA. Celebrate your success!!!

7. Lab Report:

Name: _____	Date: _____
Lab Session: _____	TA's Signature: _____

For TAs: Pre-lab (15): _____ Implementation (30+10): _____ Report (out of 45): _____
Comments: _____

Q 7. 1: Attach the files or submit them online as directed by your TA/instructor
 (ee201_GCD.v, ee201_GCD_top.v, ee201_GCD_top_Part_4_VIO.v).

Q 7. 2: What is the frequency of the clock you used in the top design to capture the value
 of the switches into registers A and B? (2 pts) _____
 Assume that whenever a user presses BtnR, he or she holds the button down for
 about 0.25 seconds. Based on this 0.25 seconds depression time, compute the
 number of times A or B values are registered at the press of the corresponding
 buttons. (6pts)



Q 7. 3: Here we used a single flip-flop (or flag) called $A_bar_slash_B$ to make it possible to
 accept A_{in} first followed by B_{in} next. To capture 16 items (item 0 to item 15), would
 you use 16 flip-flops/flags or will you be able to manage with a small counter?
 Explain. (7pts)